

ASSIGNMENT 04 – Amplifier Design

Thalagala B.P. 180631J

Note: The thermal voltage V_T is approximated to be 20 mV in the Assignment and the given set of specifications are given below.

Supply voltage V_{CC}	24V DC
Load R_L	16 Ω
Overall voltage gain $A_v = \frac{v_O}{v_{in}}$	120
Stage 1 output	Maximum voltage swing
Stage 2 output	Class A operation
Transistor 1 current gain β_1	100
Transistor 1 BE voltage V_{BE1}	0.6V
Transistor 2 current gain β_2	400
Transistor 2 BE voltage V_{BE2}	0.5V

Q1

Let the quiescent emitter current of the output leg be I_{E2} . Since we assume the **Class A operation** of the transistor Q_2 , the bias point $V_{CE2} = V_{CC}/2$.

$$\therefore I_{E2} = \frac{V_{CC}/2}{R_L} = \frac{V_{CC}}{2 \cdot R_L} = \frac{24 \text{ V}}{2 \cdot 16 \Omega} = 750 \text{ mA}$$

Q2

- Collector-emitter current ratio (α_2)

$$\alpha_2 = \frac{\beta_2}{\beta_2 + 1} = \frac{400}{400 + 1} = 0.9975$$

- Collector current (I_{C2})

$$I_{C2} = \alpha_2 \cdot I_{E2} = 0.9975 \times 750 \text{ mA} = 748.1297 \text{ mA}$$

- Transconductance (g_{m2})

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{748.1297 \text{ mA}}{20 \text{ mV}} = 37.4065 \text{ S}$$

- Intrinsic emitter resistance (r_{e2})

$$r_{e2} = \frac{\alpha_2}{g_{m2}} = \frac{0.9975}{37.4065 \text{ S}} = 0.0267 \Omega$$

Q3

Consider the voltage gain of stage 2 of the amplifier, $\frac{v_O}{v_{in2}}$. Then,

$$A_{v2} = \frac{v_O}{v_{in2}} = \frac{R_L}{r_{e2} + R_L} = \frac{16 \Omega}{16 + 0.0267 \Omega} = 0.9983$$

Q4

Let the base current of Q_2 be I_{B2} ,

$$I_{B2} = \frac{1}{\beta_2} \cdot I_{C2} = \frac{1}{400} \times 748.1297 \text{ mA} = 1.8703 \text{ mA}$$

Q5

Since $V_{BB2} = V_{BE2} + V_{R_L} = 0.5 + 12 = 12.5 \text{ V}$ and $I_{R_{B4}} = I_{B2}/9 = 1.8703 \text{ mA}/9 = 0.2078 \text{ mA}$,

$$\therefore R_{B4} = \frac{V_{BB2}}{I_{R_{B4}}} = \frac{12.5 \text{ V}}{0.2078 \text{ mA}} = 60.15 \text{ k}\Omega$$

Therefore voltage drop across R_{B3} , $V_{R_{B3}} = 24 - 12.5 = 11.5 \text{ V}$ and $I_{R_{B3}} = I_{B2} + I_{R_{B4}} = I_{B2} + I_{B2}/9 = \frac{10}{9} \cdot I_{B2} = \frac{10}{9} \times 1.8703 \text{ mA} = 2.078 \text{ mA}$.

$$\therefore R_{B3} = \frac{V_{R_{B3}}}{I_{R_{B3}}} = \frac{11.5 \text{ V}}{2.078 \text{ mA}} = 5.5338 \text{ k}\Omega$$

Q6

From the Question 03 of the Assignment 02, input resistance of stage 2 (R_{in2}) can be written as follows.

$$\begin{aligned} R_{in2} &= (R_{B3} // R_{B4}) // [(\beta_2 + 1)(r_{e2} + R_L)] \\ &= (5.5338 \text{ k}\Omega // 60.15 \text{ k}\Omega) // ((400 + 1) \times (16 + 0.0267)) \\ &= 5.0676 \text{ k}\Omega // ((400 + 1) \times (16 + 0.0267)) \\ &= 2833.3954 \Omega \end{aligned}$$

Q7

- Collector current (I_{C1}),

$$I_{C1} = \frac{1}{500} \times I_{C2} = \frac{1}{500} \times 748.1297 \text{ mA} = 1.4963 \text{ mA}$$

- Transconductance (g_{m1})

$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{1.4963 \text{ mA}}{20 \text{ mV}} = 0.0748 \text{ S}$$

Q8

Since the Overall voltage gain $A_v = \frac{v_o}{v_{in}} = 120$ and the voltage gain of stage 2 of the amplifier is $A_{v2} = 0.9983$, the required gain of stage 1 is,

$$A_{v1} = \frac{A_v}{A_{v2}} = 120/0.9983 = 120.2043$$

From the Question 05 of the Assignment 02, voltage gain of stage 1 of the amplifier can be written as follows. And therefore R_{C1} can be directly calculated from it.

$$\begin{aligned} -A_{v1} &= -g_{m1} \cdot (R_{C1} // R_{in2}) \\ 120.2043 &= 0.0748 (R_{C1} // 2833.3954 \Omega) \\ \therefore R_{C1} &= 3712.7730 \Omega \end{aligned}$$

Since Stage 1 output is specified to have a maximum voltage swing, then $V_{CE2} = V_{CC}/2 = 12 \text{ V}$. By using the result of Question 02 of the Assignment 01 and using the fact that $I_{E1} = \frac{\beta_1 + 1}{\beta_1} \cdot I_{C1}$

$$\begin{aligned} V_{CC} &= I_{C1} \cdot R_{C1} + V_{CE1} + I_{E1} \cdot R_{E1} \\ I_{E1} \cdot R_{E1} &= V_{CC} - V_{CE1} - I_{C1} \cdot R_{C1} \\ \frac{\beta_1 + 1}{\beta_1} \cdot I_{C1} \cdot R_{E1} &= V_{CC} - V_{CE1} - I_{C1} \cdot R_{C1} \\ R_{E1} &= \frac{\beta_1}{\beta_1 + 1} \times \left[\frac{V_{CC} - V_{CE1} - I_{C1} \cdot R_{C1}}{I_{C1}} \right] \\ &= \frac{100}{100 + 1} \times \left[\frac{24 \text{ V} - 12 \text{ V} - 1.4963 \text{ mA} \times 3712.7730 \Omega}{1.4963 \text{ mA}} \right] \\ &= 4264.3655 \Omega \end{aligned}$$

Q9

Let the base current of Q_1 be I_{B1} ,

$$I_{B1} = \frac{1}{\beta_1} \cdot I_{C1} = \frac{1}{100} \times 1.4963 \text{ mA} = 14.963 \mu\text{A}$$

Since the design decision has made to make $I_{RB2} = I_{B1}/9 = 14.963 \mu\text{A}/9 = 1.6626 \mu\text{A}$ and $V_{BB1} = V_{BE1} + V_{RE1} = V_{BE1} + I_{E1} \cdot R_{E1} = 0.6 + 6.4446 \text{ V} = 7.0446 \text{ V}$.

$$\therefore R_{B2} = \frac{V_{BB1}}{I_{RB2}} = \frac{7.0446 \text{ V}}{1.6626 \mu\text{A}} = 4.2374 \text{ M}\Omega$$

Therefore voltage drop across R_{B1} , $V_{RB1} = 24 - 7.0446 = 16.9554 \text{ V}$ and $I_{RB1} = I_{B1} + I_{RB2} = I_{B1} + I_{B1}/9 = \frac{10}{9} \cdot I_{B1} = \frac{10}{9} \times 14.963 \mu\text{A} = 16.6256 \mu\text{A}$.

$$\therefore R_{B1} = \frac{V_{RB1}}{I_{RB1}} = \frac{16.9554 \text{ V}}{16.6256 \mu\text{A}} = 1.0198 \text{ M}\Omega$$

Q10

From Question 04 of the Assignment 03, where V_p is the peak value of the AC signal at the load.

$$\begin{aligned}P_{L,AC} &= \frac{V_p^2}{2R_L} \\4W &= \frac{V_p^2}{2 \times 16} \\ \therefore V_p &= 8\sqrt{2} = 11.3137 \text{ V}\end{aligned}$$

Since the total gain of the amplifier is 120, peak value of the AC signal at the input is $V_p/120 = \frac{8\sqrt{2}}{120} = \frac{\sqrt{2}}{15} = 94.28 \text{ mV}$. Assume v_{in} is a pure sinusoidal signal with an angular velocity of ω then it can be written as,

$$\therefore v_{in} = 94.28 \sin(\omega.t) \text{ mV}$$

Q11

Let corresponding peak voltage at the R_L to a small signal input having a peak voltage of 85 mV be V_p . Then,

$$V_p = 85 \text{ mV} \times 120 = 10.2 \text{ V}$$

Form the Question 06 of the Assignment 03, efficiency of the output leg ($\eta_{output \text{ leg}}$),

$$\begin{aligned}\eta_{output \text{ leg}} &= \frac{V_p^2}{V_{CC}^2} \\ &= \frac{10.2^2}{24^2} \\ &= 0.180625\end{aligned}$$

$$\therefore \eta_{output \text{ leg}} = 18.0625 \%$$